

# ELP305: DESIGN AND SYSTEM LABORATORY

## EXPERIMENT 6: Design and implement GCD calculator

GROUP NUMBER: 22

EXPERIMENT DONE ON: 20/04/2018

SUBMITTED ON: 22/04/2018

SUBMITTED BY:

DRASHTI KHATSURIYA(2015MT10598)

CHARVI NAHAR(2015MT10595)

AVINASH KUMAR(2015MT10319)

**Objective:** To learn basics of ASIC design and prototyping


**Problem Statement:** Design and implement the greatest common divisor of two numbers. Design the data path of a gcd processor and construct a Moore-type state table defining the control unit of the gcd processor, an excitation table, logic equations and a complete logic circuit that uses D flip-flop and NAND gates only. Code the design in VHDL and implement on a FPGA board.

**Components required:** Xilinx Software


### Challenges Faced:



Using simple while loop for the Euclidean division algorithm to implement the GCD calculator was easy but implementing using different components like register, subtractor, multiplexer, comparator posed difficulty.



## Block Diagram:

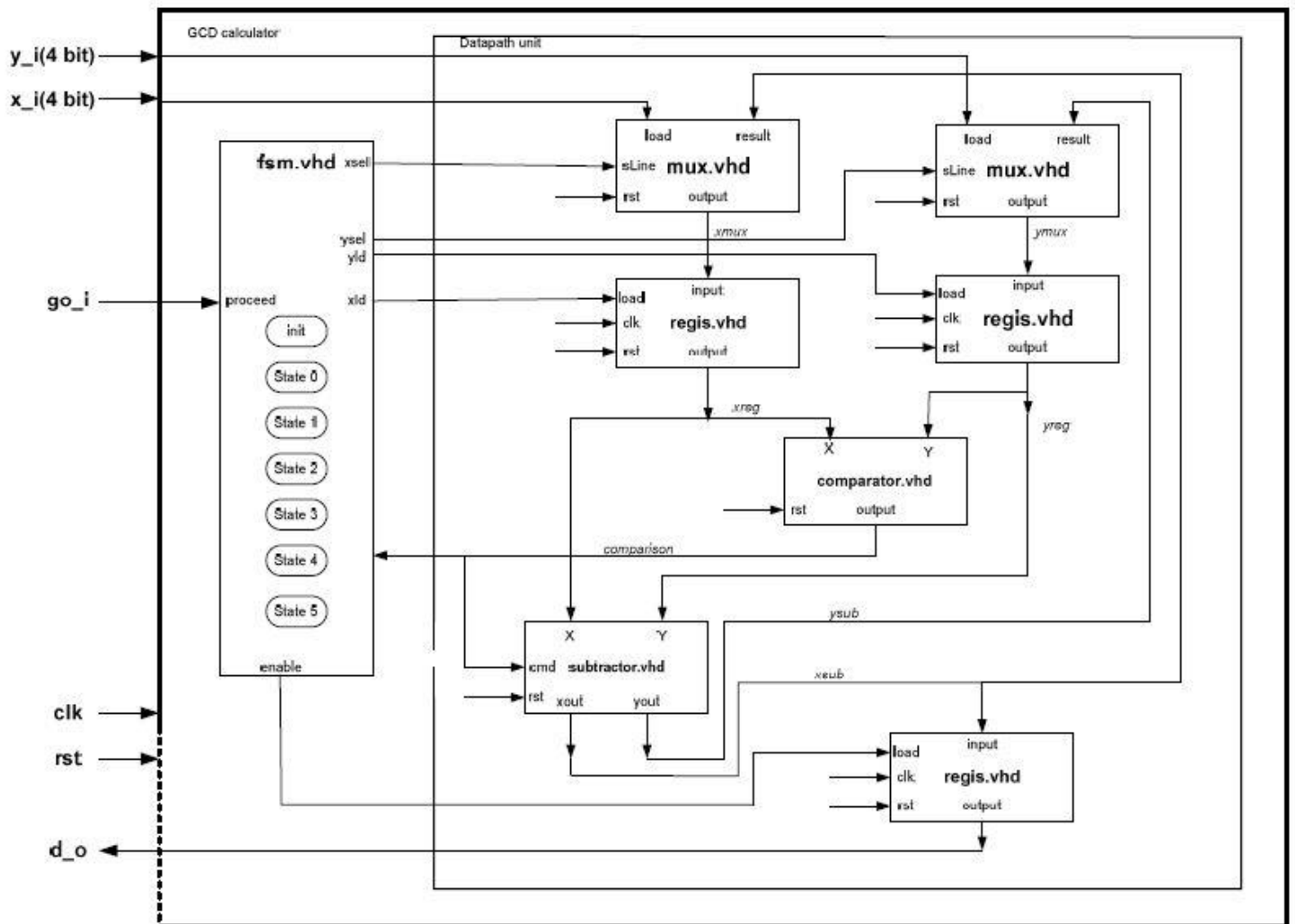


## Observations:

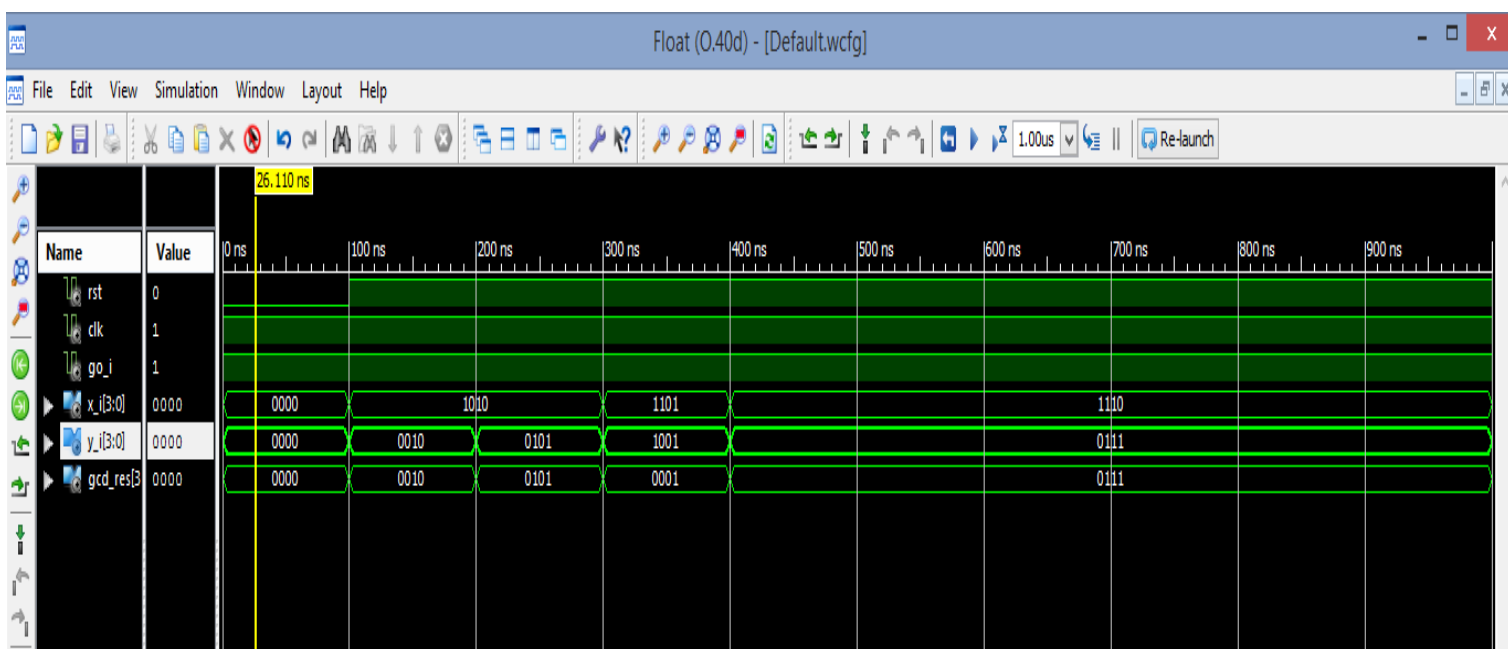

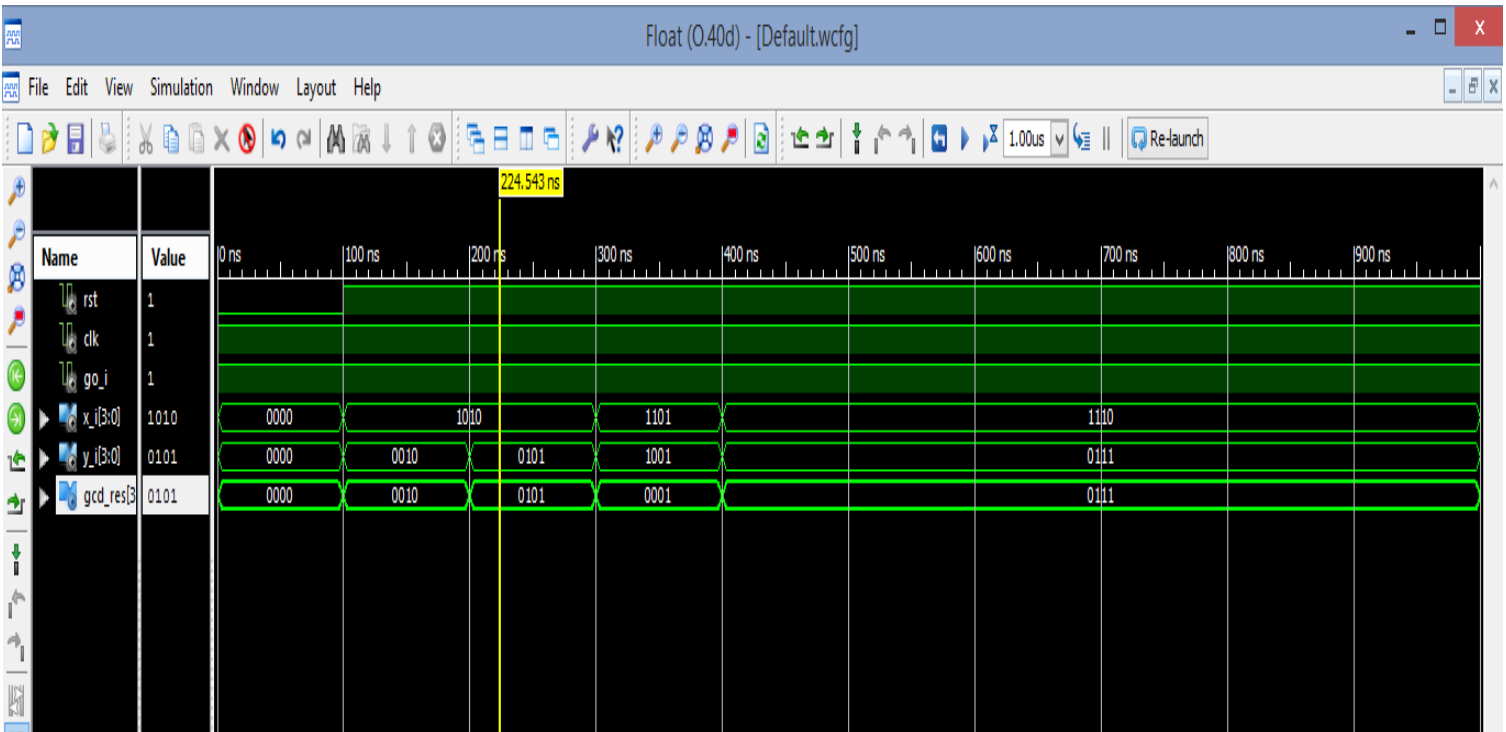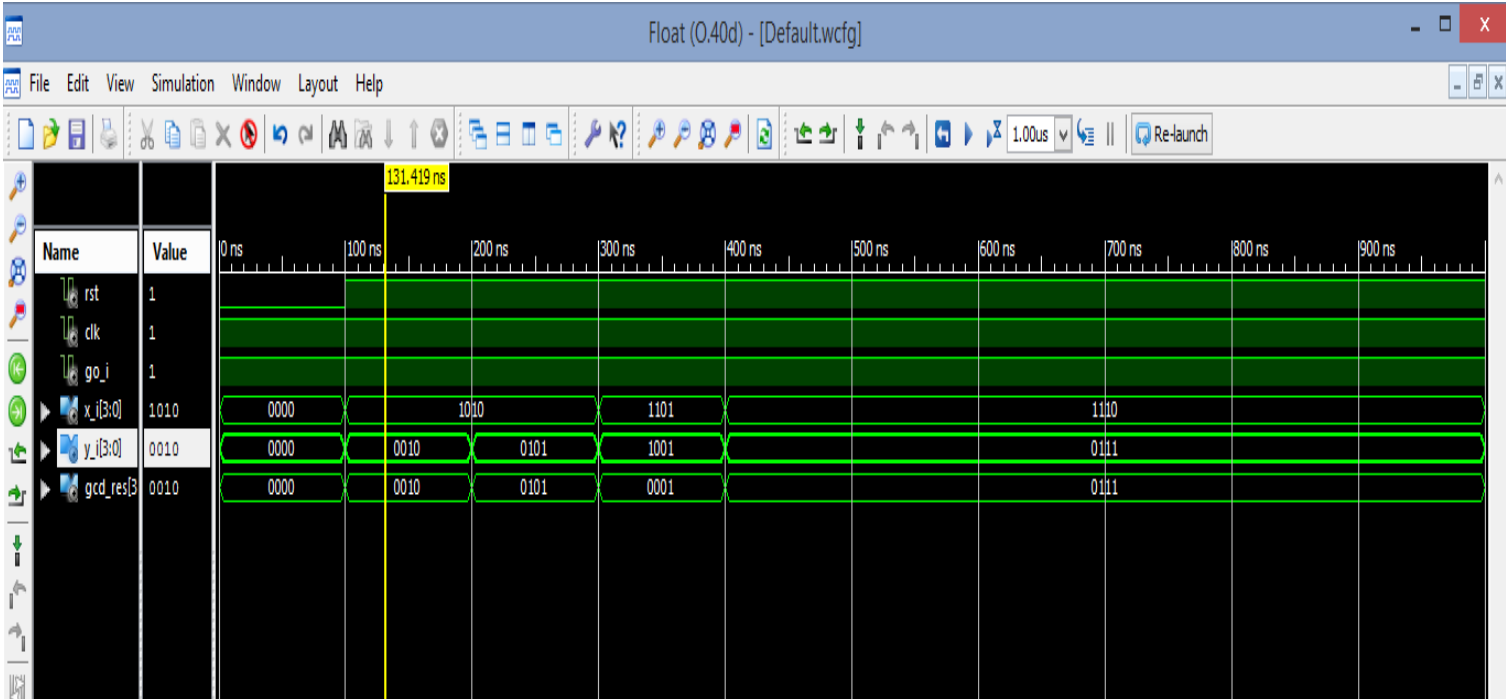

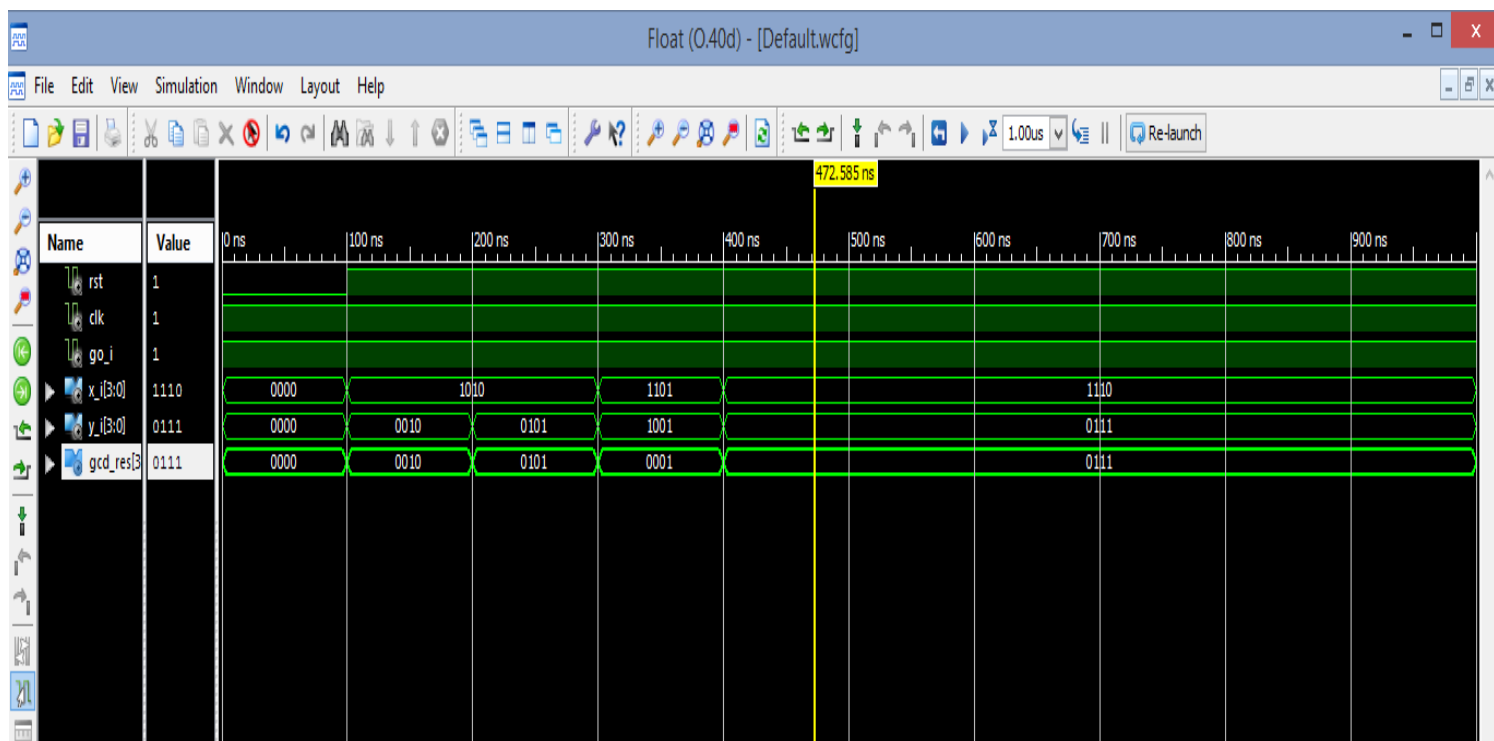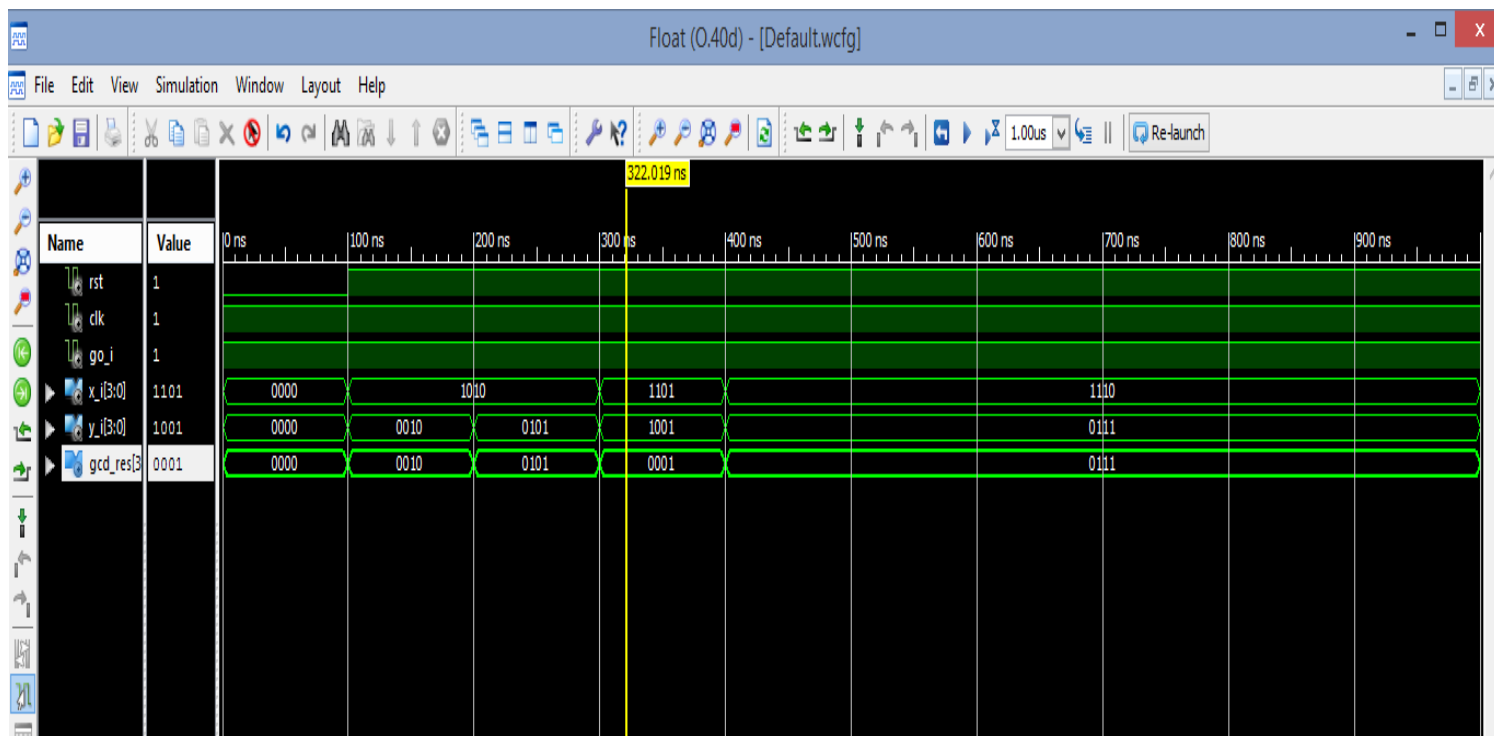

## State Diagram for code:

 

In this state diagram--

Start is: init

Input is: s0

Test1 is: s1

Update1 is: S2

Update2 is: s3

Done is: s4

## Discussion and Result:

The design of the GCD Calculator is divided into two parts: a controller and a datapath. The controller is a Finite State Machine which issues commands to the datapath based on the current state and external inputs. The datapath contains a net list of functional units like multiplexers, resistors, subtractors and a comparator and hence this design is structural. The controller steps through the GCD algorithm. If  $x=y$ , the GCD computing is finished and we go to the final state and assert the data output line. The datapath does the actual GCD computation. It has the following components:

- Mux
- Input register
- Comparator
- Subtractor
- Output register

The code implemented on the above description computes the GCD of X and Y.

## References:

<https://www.xilinx.com/itp/xilinx10/books/docs/qst/qst.pdf>

<http://esd.cs.ucr.edu/labs/tutorial/>

## Appendix (code):

### Main file:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
```

```
entity gcd is
```

```
    port( rst,clk,go_i: in std_logic;
           x_i,y_i: in std_logic_vector(3 downto 0);
           gcd_res: out std_logic_vector(3 downto 0)
         );
```

```
end gcd;
```

```
architecture gcd_arc of gcd is
```

```
    component fsm is
```

```
        port( rst,clk,proceed: in std_logic;
               comparison: in std_logic_vector(1 downto 0);
               enable,xsel,ysel,xld,yld: out std_logic
             );
```

```
    end component;
```

```
    component mux is
```

```
        port( rst,sLine: in std_logic;
```

```

        load,result: in std_logic_vector(3 downto 0);
        output: out std_logic_vector(3 downto 0)
    );
end component;

component comparator is
    port( rst: in std_logic;
          x,y: in std_logic_vector(3 downto 0);
          output: out std_logic_vector(1 downto 0)
    );
end component;

component subtractor is
    port( rst: in std_logic;
          cmd: in std_logic_vector(1 downto 0);
          x,y: in std_logic_vector(3 downto 0);
          xout,yout: out std_logic_vector(3 downto 0)
    );
end component;

component regis is
    port( rst,clk,load: in std_logic;
          input: in std_logic_vector(3 downto 0);
          output: out std_logic_vector(3 downto 0)
    );
end component;

signal xld,yld,xsel,ysel,enable: std_logic;
signal comparison: std_logic_vector(1 downto 0);
signal result: std_logic_vector(3 downto 0);

signal xsub,ysub,xmux,ymux,xreg,yreg: std_logic_vector(3 downto 0);

begin
    --- doing structure modeling here by using portmap
    --- FSM controller
    TOFSM: fsm port map(rst,clk,go_i,comparison,enable,xsel,ysel,xld,yld);

    ---Datapath
    X_MUX: mux port map(rst,xsel,x_i,xsub,xmux);
    Y_MUX: mux port map(rst,ysel,y_i,ysub,ymux);
    X_REG: regis port map(rst,clk,xld,xmux,xreg);

```

```

Y_REG: regis port map(rst,clk,yld,ymux,yreg);
U_COMP: comparator port map(rst,xreg,yreg,comparison);
X_SUB: subtractor port map(rst,comparison,xreg,yreg,xsub,ysub);
OUT_REG: regis port map(rst,clk,enable,xsub,result);

```

```

gcd_res <= result;

```

```

end gcd_arc;

```

### **Component:Mux**

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

```

```

entity mux is

```

```

    port( rst,sLine: in std_logic;
          load, result: in std_logic_vector(3 downto 0);
          output: out std_logic_vector(3 downto 0)
        );

```

```

end mux;

```

```

architecture mux_arc of mux is

```

```

begin

```

```

    process(rst,sLine,load,result)
    begin
        if(rst = '1') then
            output <= "0000";    ---do nothing
        elsif sLine = '0' then
            output <= load;      ---load inputs
        else
            output <= result;    ---load result
        end if;
    end process;

```

```

end mux_arc;

```

### **Component:Register**

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

```



entity regis is

```
    port( rst,clk,load: in std_logic;
          input: in std_logic_vector(3 downto 0);
          output: out std_logic_vector(3 downto 0)
        );
```

end regis;

architecture regis\_arc of regis is

begin

```
    process(rst,clk,load,input)
    begin
        if(rst = '1') then
            output<= "0000";
        elsif(clk'event and clk = '1')then
            if(load = '1') then
                output<= input;
            end if;
        end if;
    end process;
```

end regis\_arc;

### **Component:subtractor**

library IEEE;

use IEEE.STD\_LOGIC\_1164.all;

use IEEE.std\_logic\_arith.all;

use IEEE.std\_logic\_unsigned.all;

entity subtractor is

```
    port( rst: in std_logic;
          cmd: in std_logic_vector(1 downto 0);
          x,y: in std_logic_vector(3 downto 0);
          xout,yout: out std_logic_vector(3 downto 0)
        );
```

end subtractor;

architecture subtractor\_arc of subtractor is

begin

```
    process(rst,cmd,x,y)
    begin
        if(rst = '1' or cmd = "00") then
            xout<= "0000";
            yout<= "0000";
```

```

        elsif(cmd = "10") then
            xout<= (x-y);
            yout<= y;
        elsif(cmd="01") then
            xout<=x;
            yout<=(y-x);
        else
            xout<= x;
            yout<= y;
        end if;
    end process;
end subtractor_arc;

```

### **Component:fsm**

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

entity fsm is
    port( rst,clk,proceed: in std_logic;
          comparison: in std_logic_vector(1 downto 0);
          enable,xsel,ysel,xld,yld: out std_logic
        );
end fsm;

architecture fsm_arc of fsm is
    type states is (init,s0,s1,s2,s3,s4);
    signal nstate,cstate: states;

begin
    process(rst,clk)
    begin
        if(rst = '1') then
            cstate <= nstate;
        end if;
    end process;

    process(proceed,comparison,cstate)
    begin
        case cstate is

            when init => if(proceed = '0') then

```

```

                                nstate <= init;
                                else
                                nstate <= s0;
                                end if;

when s0 => enable <= '0';
    xsel <= '0';
    ysel <= '0';
    xld <= '1';
    yld <= '1';
    nstate <= s1;

when s1 => xld <= '0';
    yld <= '0';
    if(comparison = "10") then
        nstate <= s2;
    elsif(comparison = "01") then
        nstate <= s3;
    elsif(comparison = "11") then
        nstate <= s4;
    end if;

when s2 => enable <= '0';
    xsel <= '1';
    ysel <= '0';
    xld <= '1';
    yld <= '0';
    nstate <= s1;

when s3 => enable <= '0';
    xsel <= '0';
    ysel <= '1';
    xld <= '0';
    yld <= '1';
    nstate <= s1;

when s4 => enable <= '1';
    xsel <= '1';
    ysel <= '1';
    xld <= '1';
    yld <= '1';
    nstate <= s0;

```

```

        when others => nstate <= s0;

    end case;
end process;

end fsm_arc;

Component:Comparator
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

entity comparator is
    port( rst: in std_logic;
          x, y: in std_logic_vector(3 downto 0);
          output: out std_logic_vector(1 downto 0)
        );
end comparator;

```

```

architecture comparator_arc of comparator is
begin
    process(x,y,rst)
    begin
        if(rst = '1') then
            output <= "00";
        elsif(x>y) then
            output<= "10";
        elsif(x<y) then
            output<= "01";
        else
            output<="11";
        end if;
    end process;
end comparator_arc;

```

\*\*\*\*\*